 


# INDIAN INSTITUTE OF TECHNOLOGY KHARAGPUR

DEPARTMENT OF COMPUTER SCIENCE & ENGINEERING



## Report

Verilog Assignment-1 : Part-2

Computer Organization and Architecture Laboratory

Group No. 24

Yashraj Singh (**20CS10079**)

Vikas Vijaykumar Bastewad (**20CS10073**)

# 1. 4-bit Carry Look-ahead Adder

## Problem statement

- Design a 4-bit CLA. Clearly state, the Boolean equations of the Look-ahead carry generation for the 4 carry bits,  $C_1$ ,  $C_2$ ,  $C_3$ , and  $C_4$  in terms of the generate and propagate signals, denoted as  $G_0, \dots, G_3$  and  $P_0, \dots, P_3$  respectively. Also state the equations for the corresponding generate and propagate signals.

## Circuit Diagram

 


Figure 1: 4 bit CLA

## Description

**Boolean equations of the Look-ahead carry generation for the 4 carry bits:**

$$C_1 = G_0 + P_0 C_{in}$$

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_{in}$$

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{in}$$

$$C_{out} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_{in}$$

**Equations for the corresponding generate and propagate signals:**

for each  $i$ -th bit ( $i = 0, 1, 2, 3$ ) :

$$\text{Carry generate} \Rightarrow G_i = A_i \wedge B_i$$

$$\text{Carry propagate} \Rightarrow P_i = A_i \oplus B_i$$

## 2. Comparing the speed of 4-bit CLA with 4-bit RCA

Delay	4-bit RCA	4-bit CLA
Logic	0.249 ns	0.249
Route	1.874 ns	1.874
<b>Total</b>	<b>2.123 ns</b>	<b>2.123</b>

In the code of 4-bit CLA, we have used 'assign' function so its delay is more than expected. When we use simple gates instead of the 'assign' function, the delay will be lower as expected. Hence the delay for 4-bit Carry Look-ahead Adder will be less than 4-bit Ripple Carry Adder.

## 3. 16-bit Carry Look-ahead Adder

### (i) 4-bit Carry Look-ahead Adder (Augmented)

 


Figure 2: 4 bit CLA (Augmented)

(ii) The Hierarchical Structure of a 16-bit CLA

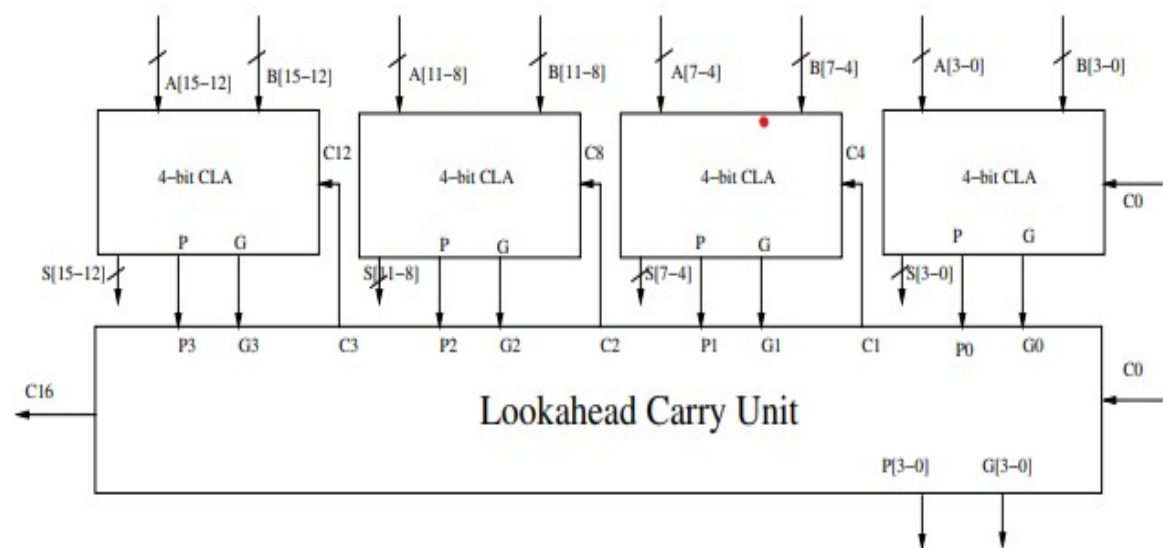


Figure 3: The Hierarchical Structure of a 16-bit CLA

(iii) 16-bit CLA (Ripple Carry out)

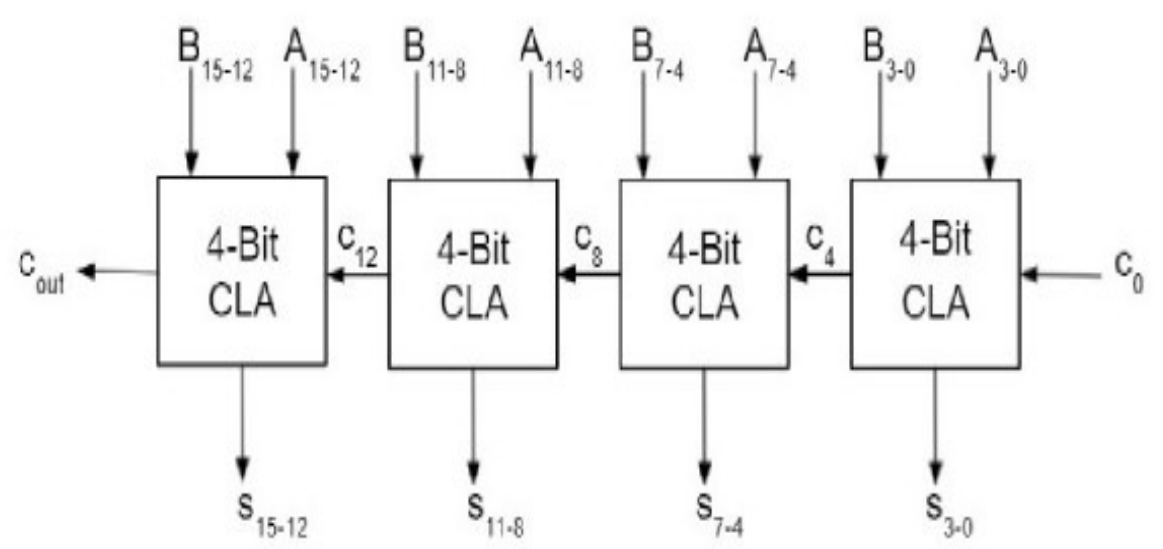


Figure 4: 16-bit CLA (Ripple Carry out)

Comparison		
	Delay	Number of Slice LUTs
16-bit CLA (Ripple carry-out)	6.197 ns	24
16-bit CLA (look-ahead carry unit)	5.513 ns	45

(iv) Speed Comparison

Comparing the 16-bit CLA with 16-bit RCA		
	Delay	Number of Slice LUTs
16-bit RCA	6.167 ns	24
16-bit CLA	5.513 ns	45

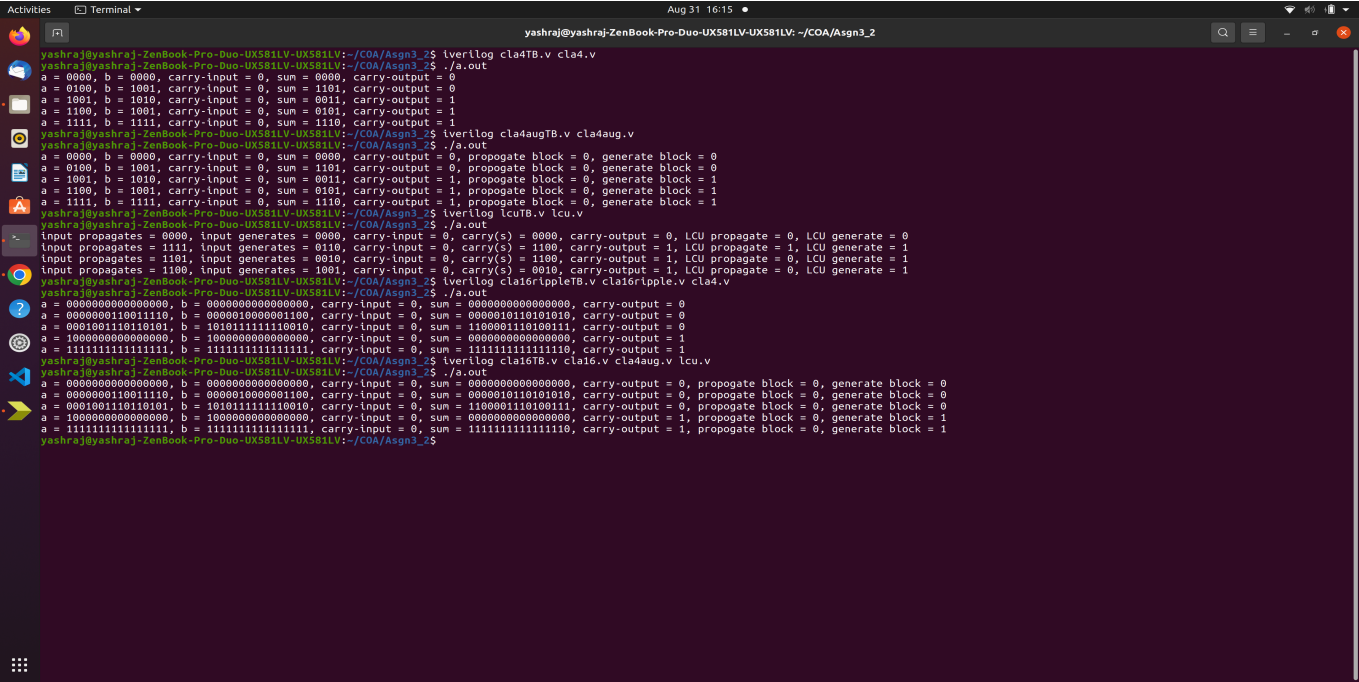


Figure 5: Output after executing Test Benches on all Verilog Files